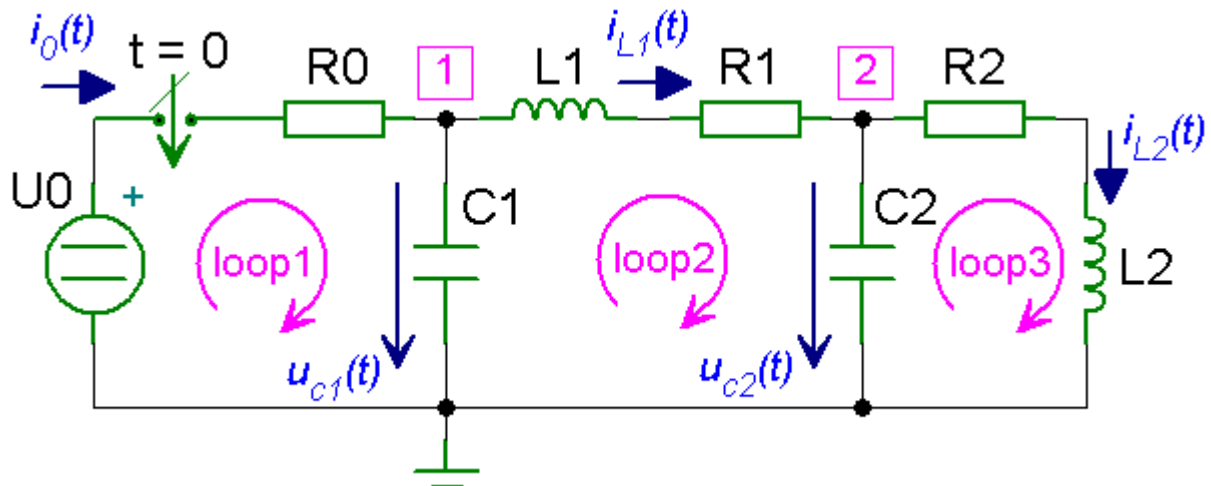


## Transient Analysis

### Example

For the circuit shown below find the currents  $i_{L1}(t)$ ,  $i_{L2}(t)$  and the voltages  $u_{C1}(t)$ ,  $u_{C2}(t)$ . Use a numerical solution to the differential equations, when  $R_0 = 100 \text{ k}\Omega$ ,  $R_1 = 300 \text{ }\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $L_1 = 0.01 \text{ mH}$ ,  $L_2 = 10 \text{ mH}$ ,  $C_1 = 10 \text{ }\mu\text{F}$ ,  $C_2 = 10 \text{ nF}$ , and  $U_0 = 10 \text{ kV}$ . The switch has been opened for a long time.



*Circuit*

### Solution

At  $t < 0$  the voltages at the capacitors are

$$u_{C1}(0) = 0 \text{ V}, \quad u_{C2}(0) = 0 \text{ V}$$

The currents flowing through the inductors are

$$i_{L1}(0) = 0 \text{ A}, \quad i_{L2}(0) = 0 \text{ A}$$

At  $t \geq 0$ , the switch is closed. Using Kirchhoff's voltage law, for the loop 1 we have

$$R_0 i_0(t) + u_{C1}(t) - U_0 = 0 \quad \Rightarrow \quad i_0(t) = \frac{U_0 - u_{C1}(t)}{R_0}$$

The other loop equations are:

$$\text{Loop 2:} \quad L_1 \frac{di_{L1}(t)}{dt} + R_1 i_{L1}(t) + u_{C2}(t) - u_{C1}(t) = 0$$

$$\text{Loop 3:} \quad R_2 i_{L2}(t) + L_2 \frac{di_{L2}(t)}{dt} - u_{C2}(t) = 0$$

Using Kirchhoff's current law and assuming that the currents leaving a node are positive, we have

For node 1:

$$-\frac{U_0 - u_{C1}(t)}{R_0} + C_1 \frac{du_{C1}(t)}{dt} + i_{L1}(t) = 0$$

At node 2:

$$-i_{L1}(t) + C_2 \frac{du_{C2}(t)}{dt} + i_{L2}(t) = 0$$

Simplifying, we get

$$\frac{di_{L1}(t)}{dt} = -\frac{R_1 i_{L1}(t)}{L_1} + \frac{u_{C1}(t)}{L_1} - \frac{u_{C2}(t)}{L_1}$$

$$\frac{di_{L2}(t)}{dt} = -\frac{R_2 i_{L2}(t)}{L_2} + \frac{u_{C2}(t)}{L_2}$$

$$\frac{du_{C1}(t)}{dt} = -\frac{i_{L1}(t)}{C_1} - \frac{u_{C1}(t)}{R_0 C_1} + \frac{U_0}{R_0 C_1}$$

$$\frac{du_{C2}(t)}{dt} = \frac{i_{L1}(t)}{C_2} - \frac{i_{L2}(t)}{C_2}$$

In matrix form, we have

$$\begin{bmatrix} \frac{di_{L1}(t)}{dt} \\ \frac{di_{L2}(t)}{dt} \\ \frac{du_{C1}(t)}{dt} \\ \frac{du_{C2}(t)}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R_1}{L_1} & 0 & \frac{1}{L_1} & -\frac{1}{L_1} \\ 0 & -\frac{R_2}{L_2} & 0 & \frac{1}{L_2} \\ -\frac{1}{C_1} & 0 & -\frac{1}{R_0 C_1} & 0 \\ \frac{1}{C_2} & -\frac{1}{C_2} & 0 & 0 \end{bmatrix} \begin{bmatrix} i_{L1}(t) \\ i_{L2}(t) \\ u_{C1}(t) \\ u_{C2}(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ \frac{U_0}{R_0 C_1} \\ 0 \end{bmatrix}$$

The MATLAB program for solving the above differential equations in the interval  $0 \leq t \leq 500$  ms is

### ***MATLAB Script***

```
function transient_analysis_03
% Transient analysis of RLC circuit using ode function
ts=0;      % start time
te=0.5;    % end time
x0=[0 0 0 0]; % initial conditions
[t,x]=ode23t(@diffeq,[ts te],x0);
% plot iL1(t)
subplot(4,1,1); plot(t,x(:,1));
xlabel('t [s]'); ylabel('iL1(t) [A]'); grid on;
% plot iL2(t)
subplot(4,1,2); plot(t,x(:,2));
xlabel('t [s]'); ylabel('iL2(t) [A]'); grid on;
% plot uC1(t)
subplot(4,1,3); plot(t,x(:,3));
xlabel('t [s]'); ylabel('uC1(t) [V]'); grid on;
% plot uC2(t)
subplot(4,1,4); plot(t,x(:,4));
xlabel('t [s]'); ylabel('uC2(t) [V]'); grid on;
% differential equations
function dxdt=diffeq(t,x)
R0=100e+3; R1=300; R2=10e+3;
L1=0.01e-3; L2=10e-3;
C1=10e-6; C2=10e-9;
U0=10e+3;
A=[ -R1/L1      0      1/L1      -1/L1;
     0      -R2/L2      0      1/L2;
    -1/C1      0     -1/(R0*C1)      0;
     1/C2     -1/C2      0      0 ];
F=[0; 0; U0/(R0*C1); 0];
dxdt=A*[x(1); x(2); x(3); x(4)]+F;
```

Notice:

If you used the function ode23, the computation of this task would be very time-consuming. Therefore the function ode23t has been used.

The plots obtained from MATLAB are

