


## Frequency Response

### Example

For the circuit shown below find the transfer function

$$H(s) = \frac{U_R(s)}{U_S(s)}$$

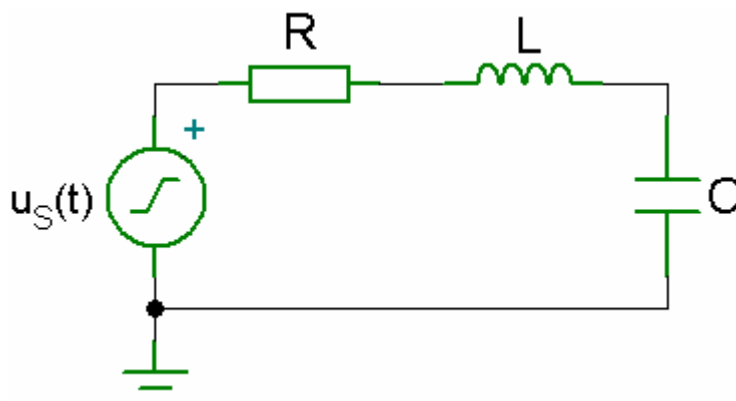and with using MATLAB plot the frequency response of the transfer function  $H(s)$  when  $R = 10 \text{ k}\Omega$ ,  $L = 5 \text{ H}$ ,  $C = 1.12 \text{ }\mu\text{F}$ . What happens when  $R = 100 \text{ }\Omega$ , but  $L$  and  $C$  remain unchanged?



*RLC Circuit*

### Solution

The voltage  $U_R(s)$  is

$$U_R(s) = U_S(s) \frac{R}{R + sL + \frac{1}{sC}}$$

Thus the frequency response is

$$H(s) = \frac{U_R(s)}{U_S(s)} = \frac{R}{R + sL + \frac{1}{sC}} = \frac{RCs}{LCs^2 + RCs + 1}$$

The answer to the question mentioned above can be found in the MATLAB results.

The MATLAB program for solving this task is

### ***MATLAB Script***

```
% Frequency response of RLC filter
clear; clc; R1=10000; R2=100; L=5; C=1.12e-6;
numerator1 = [R1*C 0]; denominator1 = [L*C R1*C 1];
w = logspace(1,4); f = w/(2*pi);
h1 = freqs(numerator1,denominator1,w);
mag1 = abs(h1); phase1 = angle(h1)*180/pi;
numerator2 = [R2*C 0]; denominator2 = [L*C R2*C 1];
h2 = freqs(numerator2,denominator2,w);
mag2 = abs(h2); phase2 = angle(h2)*180/pi;
subplot(2,2,1); loglog(f,mag1);
title('Magnitude response R = 10000 Ohms');
xlabel('frequency [Hz]'); ylabel('magnitude');
subplot(2,2,2); loglog(f,mag2);
title('Magnitude response R = 100 Ohms');
xlabel('frequency [Hz]'); ylabel('magnitude');
subplot(2,2,3); semilogx(f,phase1);
title('Phase response R = 10000 Ohms');
xlabel('frequency [Hz]'); ylabel('angle in degrees');
subplot(2,2,4); semilogx(f,phase2);
title('Phase response R = 100 Ohms');
xlabel('frequency [Hz]'); ylabel('angle in degrees');
```

The plots obtained from MATLAB are

